

物理实验教学中心

Physics Experiment Center




Wheatstone Bridge

Li Bin
NJUPT

I. Purposes


1. Know the structure and measurement principles of Wheatstone Bridge.
2. Build the circuit and handle the method of measuring resistance.

II. Principles

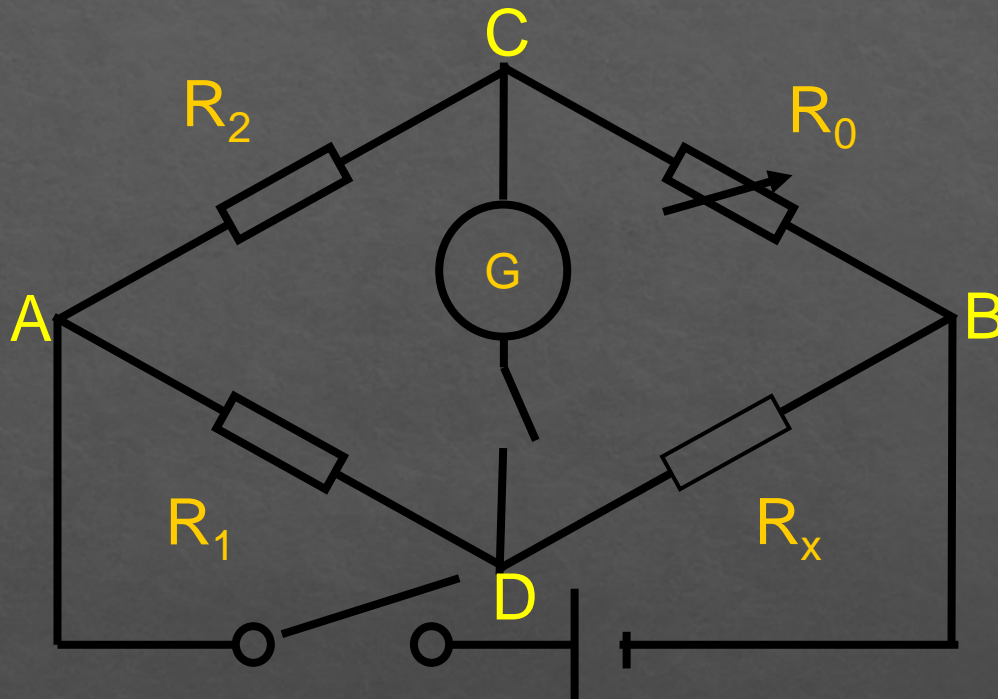

If $I_G = 0$,
$$R_x = \frac{R_1}{R_2} R_0$$

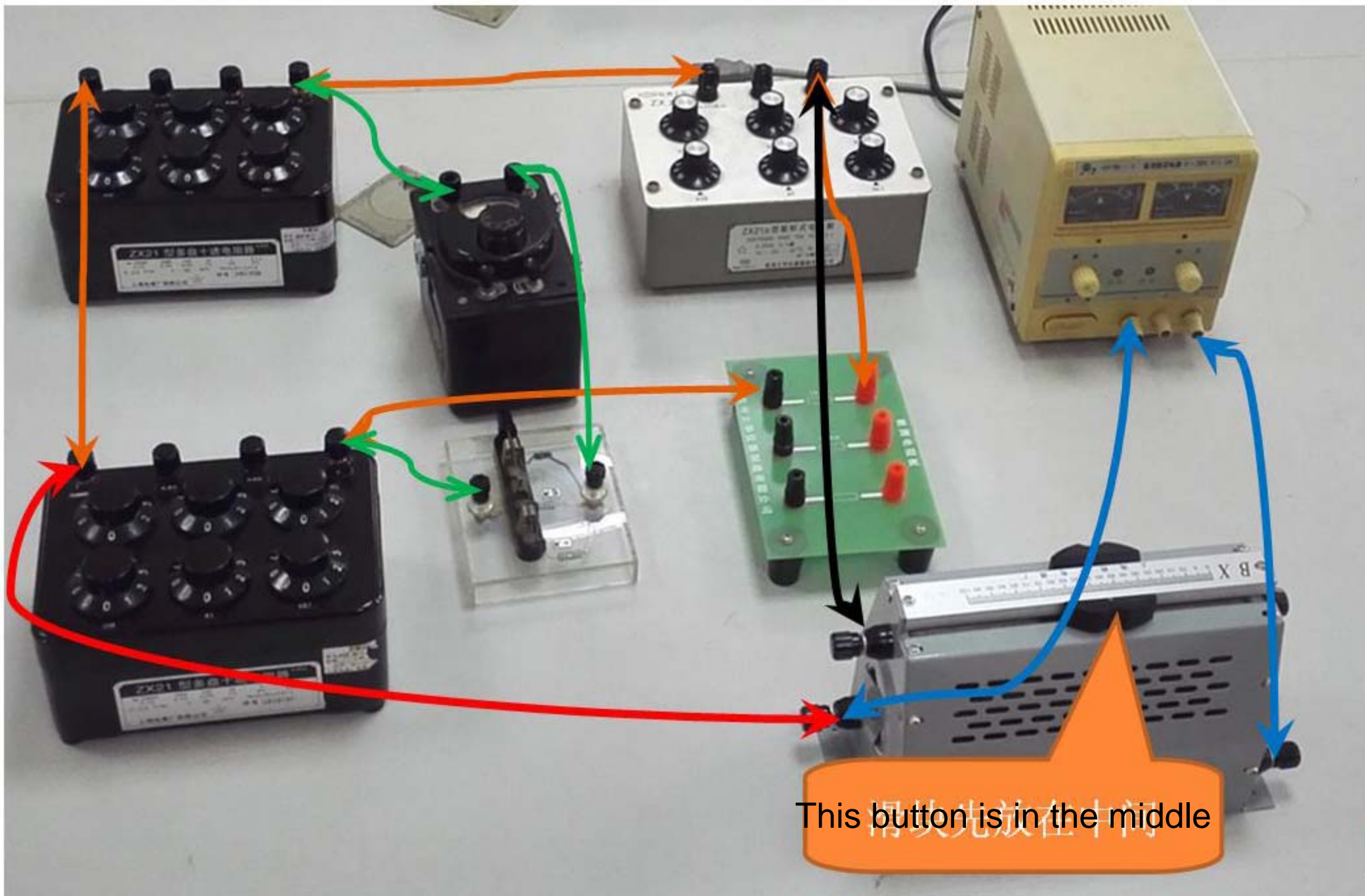Bridge sensitivity: $S = \Delta n / (\Delta R_0 / R_0)$



Galvanometer


Zero adjustment

Safe switch,
turn to
white point

Break off

Switch
on

Source

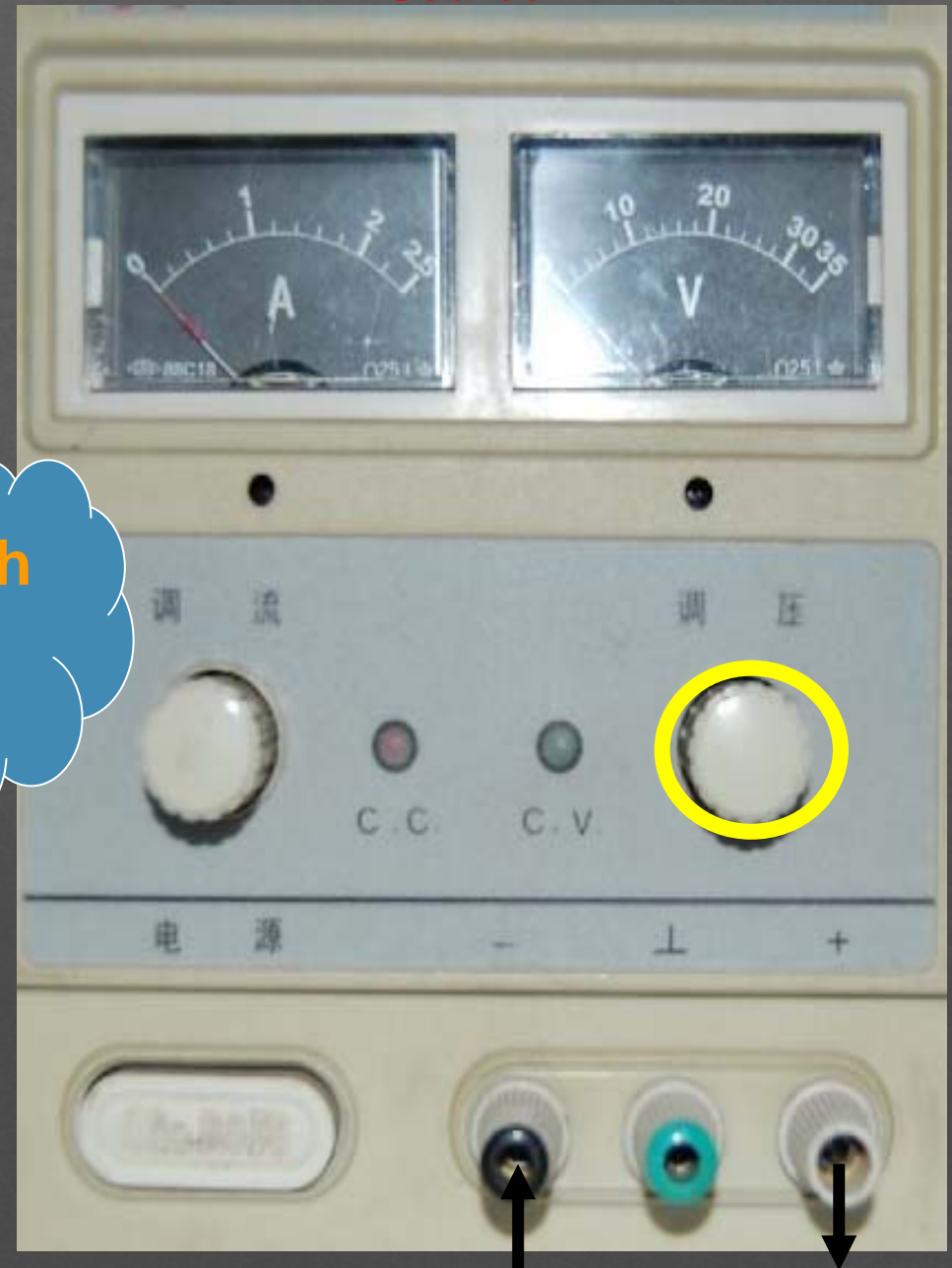

III. Contents and Steps

1. Connect the circuit;

2. Initialize the instruments, Set the ratio: R_1/R_2 ,

$R_{x1} \sim 30 \Omega \longrightarrow R_1 : R_2 = 100.0 : 1000.0$
and $100.0 : 2000.0$

$R_{x2} \sim 1500 \Omega \longrightarrow R_1 : R_2 = 1000.0 : 1000.0$
and $1000.0 : 2000.0$

3. Coarse adjustment: open switch S_g , adjust R_0 to make $I_g=0$;

4. Fine adjustment: close S_g , adjust R_0 again to make $I_g=0$;

5. Bridge sensitivity measurement: after $I_g=0$, continue to change R_0 , let the indicator deviate from the equilibrium position five grids ($\Delta n=5$), record the new value of R_0 and calculate ΔR_0 ;

6. Change R_1/R_2 , repeat step 3-5.

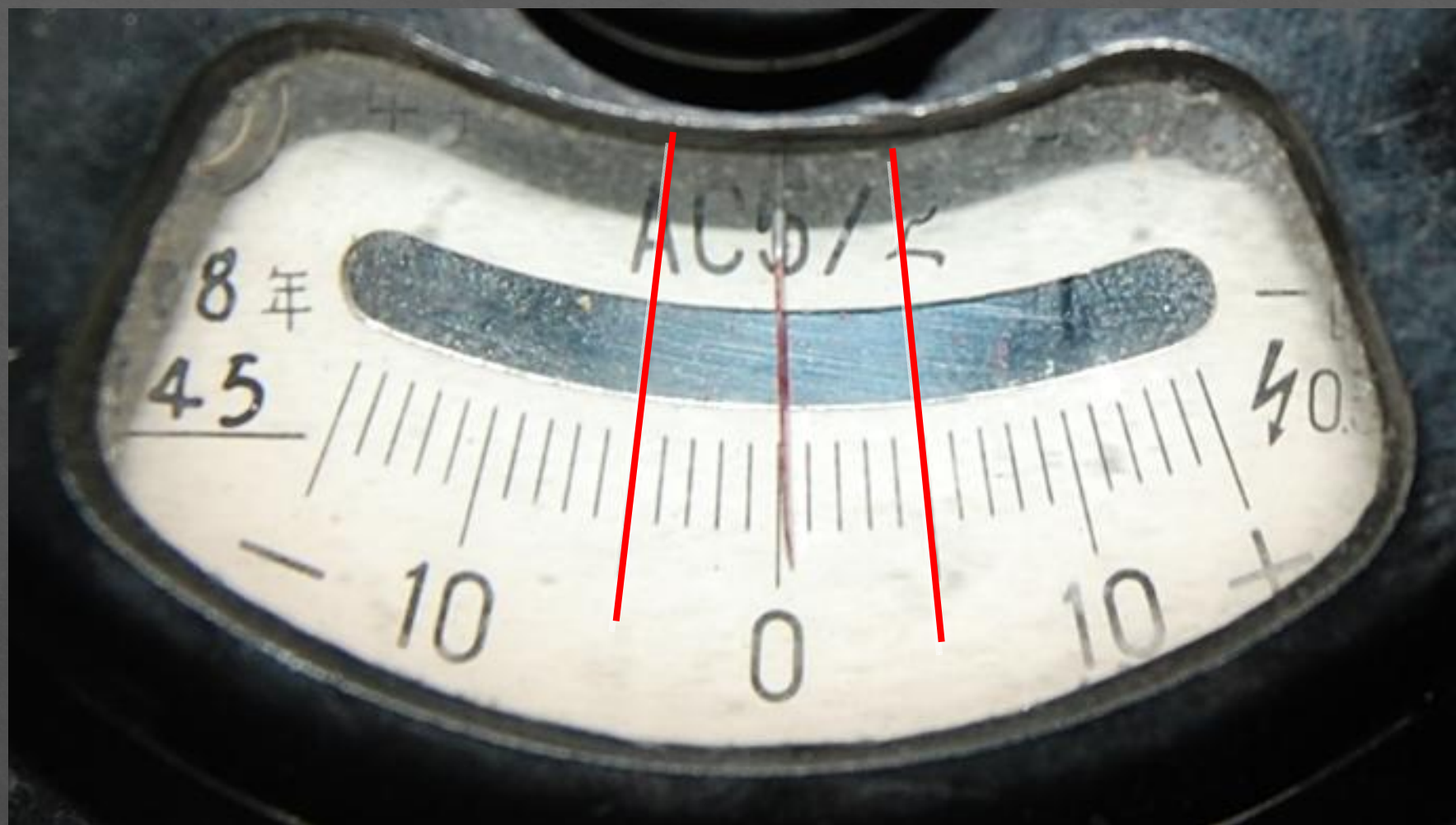


Table I

No. \ R	R_1/Ω	R_2/Ω	R_0/Ω	R_{x1}/Ω	$\Delta R_0/\Omega$
1	100	1000			
2	100	2000			

Table II

No. \ R	R_1/Ω	R_2/Ω	R_0/Ω	R_{x2}/Ω	$\Delta R_0/\Omega$
1	1000	1000			
2	1000	2000			

END