

物理实验教学中心

Physics Experiment Center



Measurement of electrodynamic potential using 11-cord potential difference meter


Li Bin

NJUPT

Purposes:

1. Know the compensation method.
2. Learn to use 11-cord potential difference meter
3. Measure the electrodynamic potential (electric voltage).

Circuit Diagram

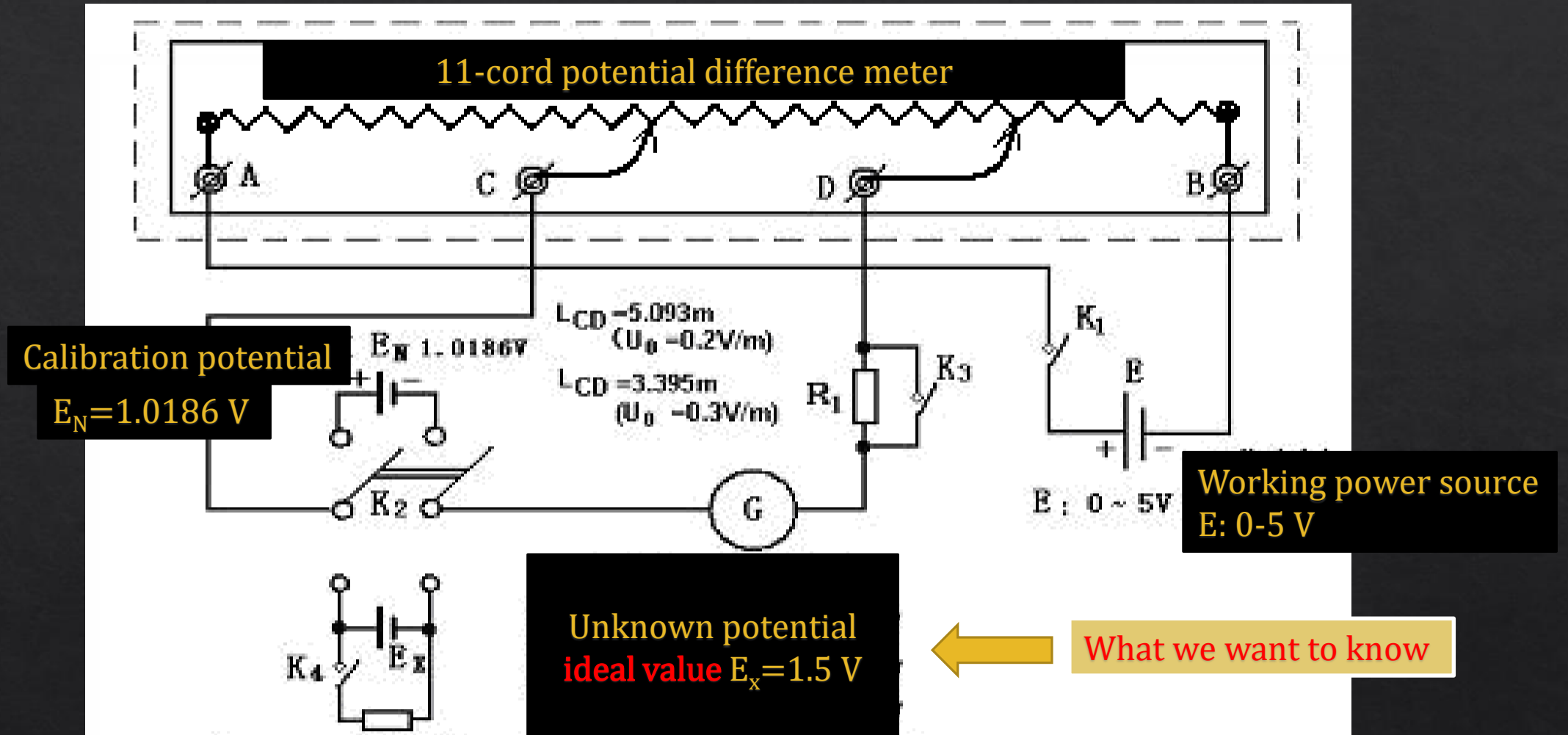

$E_N = U_{CD} = U_0 * L_{CD}$, U_0 is called **correction factor**, L_{CD} is the length of the resistance wire between C & D.
 $E_x = U_{CDx} = U_0 * L_{CDx}$. E_N is known, if we know L_{CD} and L_{CDx} , we can obtain E_x .

◊ $E_N = U_{CD} = U_0 * L_{CD}$, U_0 is called **correction factor**, L_{CD} is the length of the resistance wire between C & D.

◊ $E_x = U_{CDx} = U_0 * L_{CDx}$. E_N is known, if we know L_{CD} and L_{CDx} , we can obtain E_x .



Steps:

1. Connect circuit;
2. Galvanometer zero adjustment;
3. Calculate L_{CD} for correction factor $U_0 = 0.2 \text{ V/m}$, using $L_{CD} = E_N/U_0 = 1.0186/0.2 = 5.093 \text{ m}$;
4. Regulate the length of CD to L_{CD} , adjust the voltage to make galvanometer displaying 0 at 10^{-8} gear;
5. Calculate the ideal L_{CDx} for correction factor $U_0 = 0.2 \text{ V/m}$, using $L_{CDx} = E_x/U_0 = 1.5/0.2 = 7.5 \text{ m}$;
6. Keep the voltage unchanged, adjust the length of CD to make galvanometer displaying 0 at 10^{-8} gear. Record the measured L_{CDx} ;
7. Calculate the actual value of $E_x = L_{CDx} * U_0$;
8. Change U_0 to 0.3 V/m , redo 3-7 steps.

U_0 /(V/m)	E (voltmeter) /V	L_{CD} (calculated) /m	L_{CDx} (measured) /m	E_x /V
0.2				
0.3				

$$E_x = L_{CDx} * U_0$$

END