

# 物理实验数学中心

Physics Expeiment Center



# Measuring low-resistances using double bridge

Li Bin


**NJUPT** 

# Experiment purposes


- > Know the meaning of four probe method and structure of double bridge;
- Learn to use double bridge to measure low resistance;
- > Learn to measure resistivity of conductor

### Principles

Four Probe Method

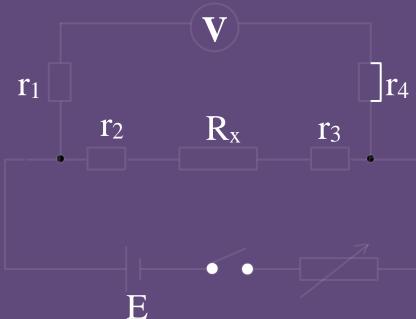

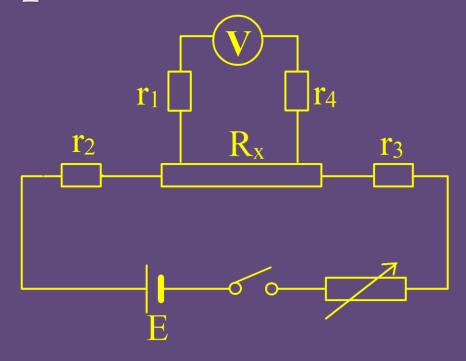Measuring resistance
 using Voltammetry,
 contact resistance,
 conductor resistance, If r<sub>2</sub>
 and r<sub>3</sub>>=R<sub>x</sub>, we can not
 use this circuit to measure




low resistance R<sub>X</sub>->two
Current contact C-C,
two Voltage contact P-P.
Four-Probe Method

Van der Pauw Method

 $R_{x}$   $\circ$ 

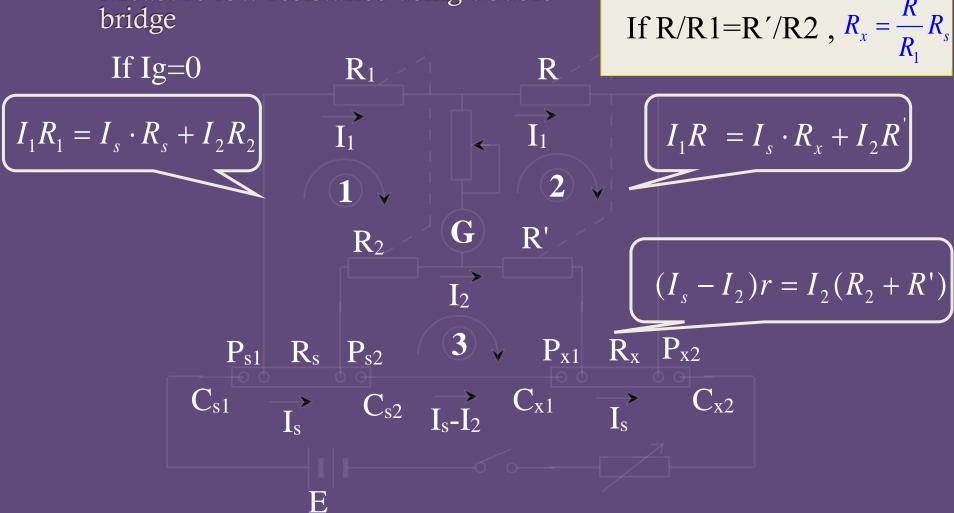Measure low resistance using double bridge




$$R_{x} = \frac{R}{R_{1}}R_{s} + \frac{r \cdot R_{2}}{r + R^{'} + R_{2}}(\frac{R}{R_{1}} - \frac{R^{'}}{R_{2}})$$

#### > Experimental apparatus



#### **Operation**

#### 1. Circuit diagram

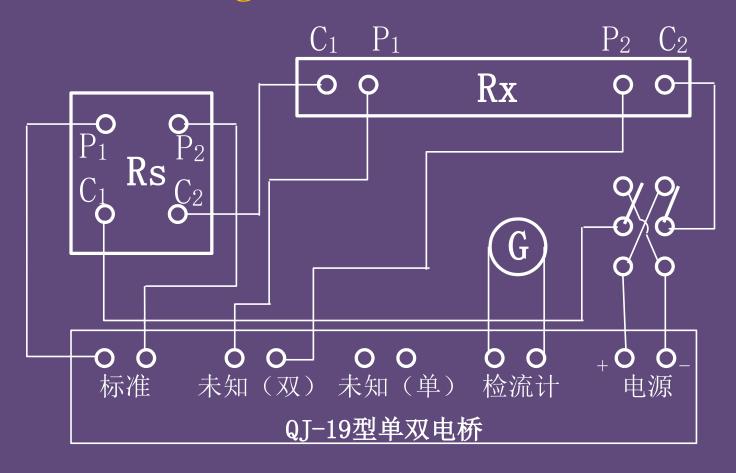

### 2. Initial adjustment

adjustment of double bridge



Switch to "double bridge" (双桥)

# adjustment of galvanometer

Galvanometer
switch gear-> "zeroadjustment (调
零) ",turn the
zero-adjustment
knob to adjust



After zeroadjustment, switch gear-> maximum range "30mV"


### **♦** Adjustment of standard resistance



Generally, standard resistance -> " $0.1\Omega$ " . According to the actual situation to make corresponding adjustments during measurement. The selected principle: double bridge: 5 effective number, no more than the measurement range of double bridge.
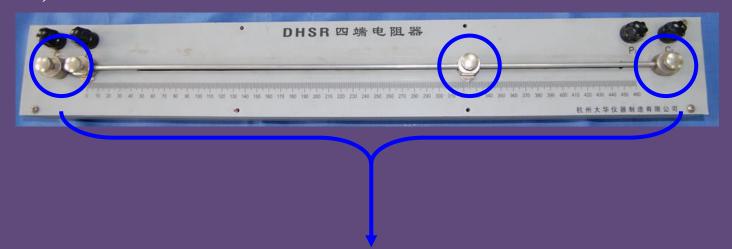
## **♦** Adjustment of resistance

By adjusting the slider to select resistance's length to be measured, choose two lengths (200mm, 400mm) to measure.



Notes: to ensure good contact with metal rods, tightening knobs during experiment.

#### 3. Measurements (take 200mm copper rod as an example)

- ① insert copper bar at four terminal resistance box, adjusting the sliding side to 200mm.
- ② After zero-adjustment, switch gear-> maximum range "30mV"
- 3 Turn off reversing switch, adjust double bridge, Make the galvanometer indicated as *zero*, adjust double bridge.
- 4 Adjust the galvanometer to "3mV", adjust double bridge once more, make the galvanometer indicated as zero. Adjust gradually until galvanometer-> " $30\mu V$ ", Balance indicator->0. Record R resistance of double bridge .
- ⑤ Turn the reversing switch to the other side, backward current, adjust bridge balance once more according to ③、④, record R.

Table I: Diameters of the copper rod

NO.	1	2	3	4	5	Average d
d (mm)						

#### Table II: Resistance and resistivity

 $R1=R2=10000 \Omega$ 

	L	$R_{\rm S}$	R		$\overline{D}$	D	O	$\left  \frac{1}{2} \right $
	(mm)		+	-	R	$\kappa_{\rm X}$		
Copper	200	0.01						
Copper rod	400	0.1						

$$R_{x} = \frac{R}{R_{1}}R_{s}, R1 = 100000;$$

 $\rho = \pi d^2 R_x/4L$ , d: diameter of copper rod,L:length of rod(200mm,400mm);

$$U_{\rho} = \rho. \sqrt{(\frac{U_{R_{x}}}{R_{x}})^{2} + 4(\frac{U_{d}}{\overline{d}})^{2} + (\frac{U_{L}}{L})^{2}}; \frac{U_{R_{x}}}{R_{x}} = 0.005, U_{L} = 1mm,$$

$$U_d = \sqrt{{U_A}^2 + {U_B}^2}, U_A = s.\frac{t}{\sqrt{n}}, U_B = 0.004mm, (\frac{t}{\sqrt{n}} = 1.24, s = \sqrt{\frac{\sum (d_i - \overline{d})^2}{n - 1}}, n = 5)$$

Here is the weblink to download this slide:

https://github.com/bliseu/phylab/

Some useful links:

https://www.elprocus.com/what-is-a-kelvin-double-bridge-and-its-working/

https://circuitglobe.com/kelvin-bridge.html

https://www.sciencedirect.com/science/article/abs/pii/004060909490863X#:~:text=The% 20Van%20der%20Pauw%20method%20is%20one%20of,the%20given%20graph%20was%20confirmed%20by%20numerical%20calculations.

- 1. Please calculate and finish the tables in the slide, compare the calculated resistivity of copper with the theoretical value.
- 2. A 500-word description of the "Double-Bridge Method" and "Van der Pauw Method" should be given in the report.

The DEADLINE is May 30, 2024.

# END